

## DDCO Mini Project ISA Submission


**Project Title: Sequence Generator (Even number generator)**

**Section : H**

**Batch Details**

Student Name	SRN
SUHAS R K	PES1UG19CS514
SUHEB PAPA	PES1UG19CS515
SUJAY S AMBEKAR	PES1UG19CS516
SUJAY S SHIVARA	PES1UG19CS517

**Circuit Diagram:**

 

**Algorithm (if any):**

Since all even numbers in binary ends with 0's,

To construct an n-bit even number generator.

We implement an n-1 bit counter and have a constant LSB output of 1'b0.

For a 4 bit even number generator:

The counter is made of 3 d-flip flops and with one reset, an incrementer circuit and one grounded wire for LSB of output.

**Implementation (Code):****TESTBENCH:**

```
`timescale 1 ns / 100 ps
```

```
module tb;
```

```
    // Initialising clock, reset, output wires and even sequence generator module
```

```
    wire [ 3 : 0 ] out;
```

```
    reg clk, reset;
```

```
    even_seq_gen s_g0 (clk, reset, out);
```

```
    // Generating a dump file and the dump variable
```

```

initial begin

    $dumpfile ( "tb_even_seq_gen.vcd" );

    $dumpvars ( 0 ,tb);

end


// executing the even sequence generator module


initial begin

    reset = 1'b1 ;

    #10 reset = 1'b0 ;

end

initial clk = 1'b0 ;

always #5 clk =~ clk;

initial #300 $finish ;

endmodule

```

## **MODULES:**

```

module invert(input wire ip, output wire out);

    assign out = ! ip;

endmodule


module and2(input wire ip0, ip1, output wire out);

    assign out = ip0 & ip1;

endmodule

```

```
module xor2(input wire ip0, ip1, output wire out);  
    assign out = ip0 ^ ip1;  
endmodule
```

```
module and3(input wire ip0, ip1, ip2, output wire out);  
    wire t;  
    and2 and2_0 (ip0, ip1, t);  
    and2 and2_1 (ip2, t, out);  
endmodule
```

```
module df(input wire clk, in, output wire out);  
    reg df_out;  
    always @(posedge clk) df_out <= in;  
    assign out = df_out;  
endmodule
```

```
module dfr(input wire clk, reset, in, output wire out);  
    wire reset_, df_in;  
    invert invert_0 (reset, reset_);  
    and2 and2_0 (in, reset_, df_in);  
    df df_0 (clk, df_in, out);  
endmodule
```

```
module even_seq_gen(input wire clock, reset, output wire [3:0]out);  
    assign out[0] = 1'b0 ;  
    wire s1, s2, s3, c1;  
  
    invert i_0 (out[1], s1);  
    xor2 x_0 (out[2], out[1], s2);  
    and2 a_0 (out[2], out[1], c1);  
    xor2 x_1 (c1, out[3], s3);  
  
    dfr d_0 (clock, reset, s1, out[1]);  
    dfr d_1 (clock, reset, s2, out[2]);  
    dfr d_2 (clock, reset, s3, out[3]);  
endmodule
```

## Output:

